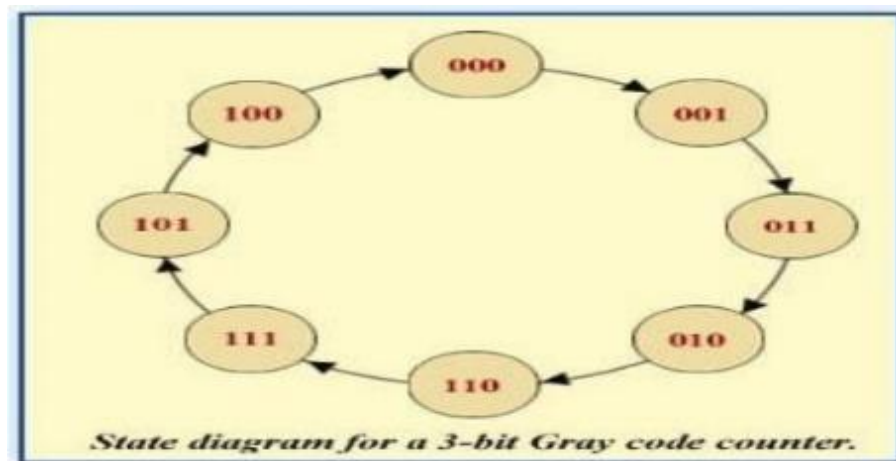


CS 220 ASSIGNMENT 4

1. State Assignment Table:

<i>Sr. No.</i>	<i>State Name</i>	<i>State</i>
1.	S ₀	1'b000
2.	S ₁	1'b001
3.	S ₂	1'b011
4.	S ₃	1'b010
5.	S ₄	1'b110
6.	S ₅	1'b111
7.	S ₆	1'b101
8.	S ₇	1'b100

2. State Diagram:




Output is high only when state transits from S₇ to S₀.

Elsewhere output is low.

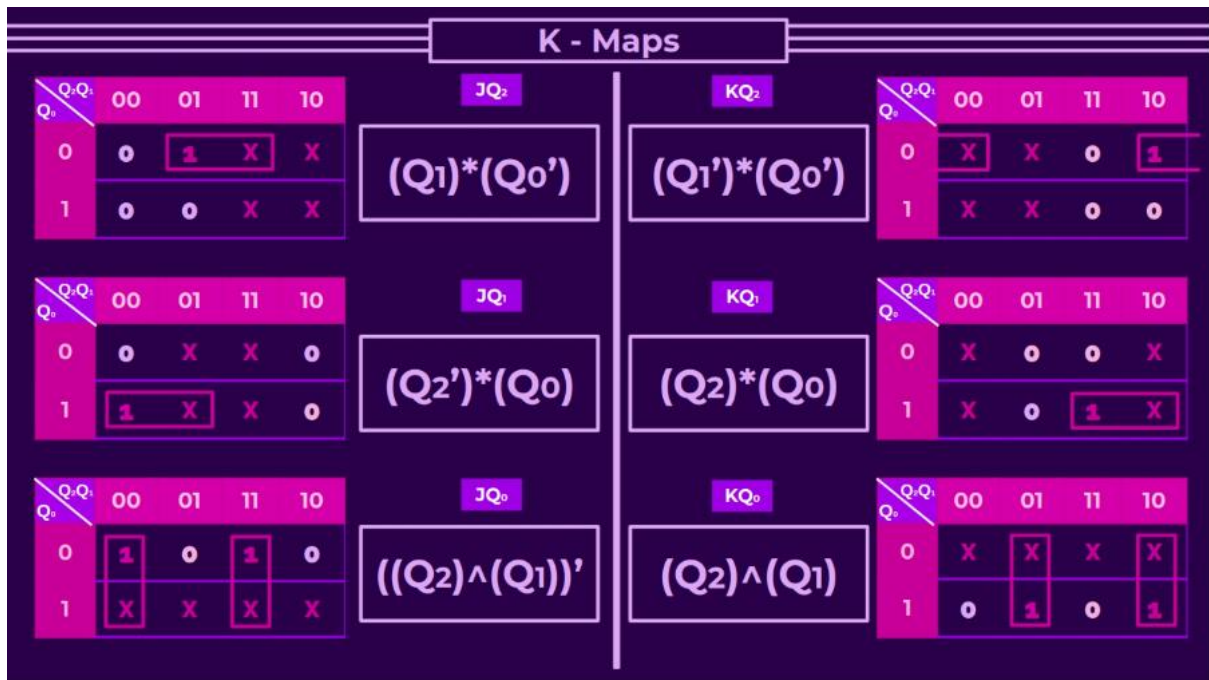3. Karnaugh Maps and logic Equations:

K-Maps for the Gray code Counter is given below. The circuit consists of 3 J-K Flip-flop and thus the K-Maps corresponds to the 6 J and K values of the three Flip-flops.

The Logic Equation corresponding to each output is also given below.



Note: Here JQ_2 , JQ_1 , etc. means J or K outputs of the corresponding Flip-flop 0, 1 or 2.


Cross means don't care condition.

4. J-K Transition Table:

$Q(t+1) = J.Q'(t) + K'.Q(t)$

Trigger	Inputs		Output				Inference
			Present State		Next State		
CLK	J	K	Q	Q	Q	Q	
X	x	x	-		-		Latched
↑	0	0	0	1	0	1	No Change
↑			1	0	1	0	
↑	0	1	0	1	0	1	Reset
↑			1	0	0	1	
↑	1	0	0	1	1	0	Set
↑			1	0	1	0	
↑	1	1	0	1	1	0	Toggles
↑			1	0	0	1	

5. Circuit Diagram:

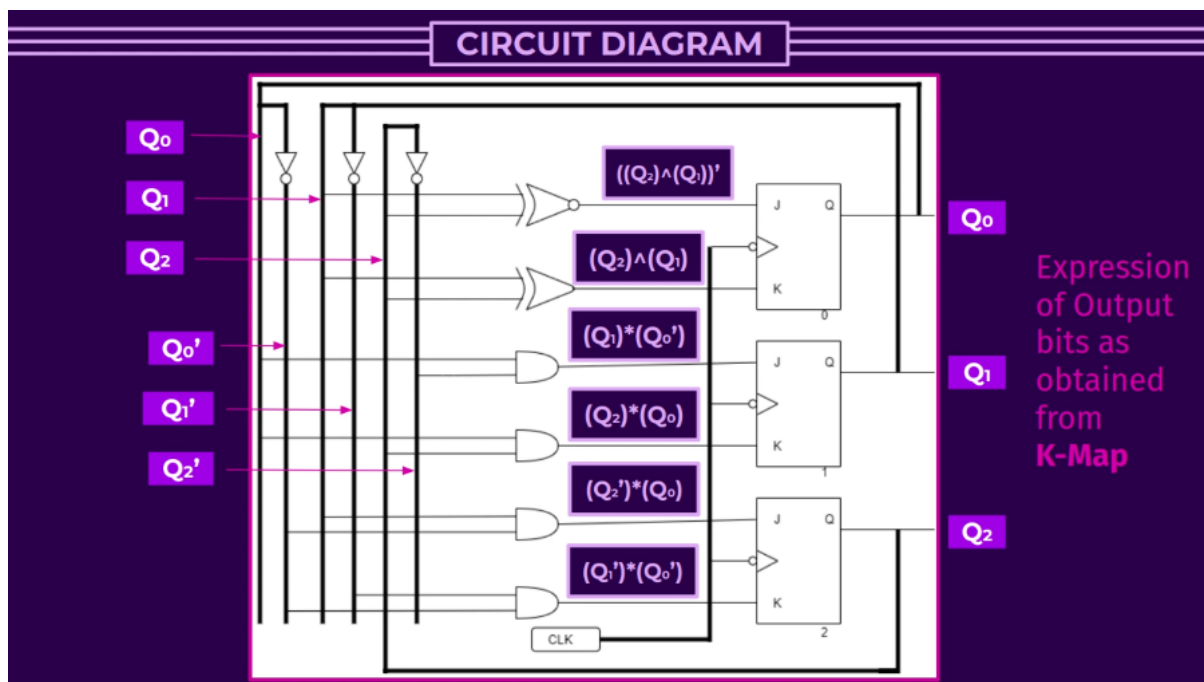

6. Output Table:

Sr. No.	Clock	State	Output (z)
1.	High	S ₀	0
2.	Low		0
3.	High	S ₁	0
4.	Low		0
5.	High	S ₂	0
6.	Low		0
7.	High	S ₃	0
8.	Low		0
9.	High	S ₄	0
10.	Low		0
11.	High	S ₅	0
12.	Low		0
13.	High	S ₆	0
14.	Low		0
15.	High	S ₇	1
16.	Low		0

7. State and Excitation Table:

Current State	Next State	Output
S ₀	S ₁	0
S ₁	S ₂	0
S ₂	S ₃	0
S ₃	S ₄	0
S ₄	S ₅	0
S ₅	S ₆	0
S ₆	S ₇	0
S ₇	S ₀	1